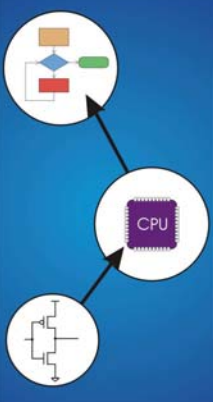




Introduction to Computer Engineering

ECE/CS 252, Fall 2008
 Prof. Mikko Lipasti
 Department of Electrical and Computer Engineering
 University of Wisconsin – Madison



Chapter 3

Digital Logic Structures

Slides based on set prepared by
 Gregory T. Byrd, North Carolina State University

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Transistor: Building Block of Computers

Microprocessors contain millions of transistors

- Intel Core 2 Duo: 291 million
- AMD Barcelona: 463 million
- IBM Power6: 790 million

Logically, each transistor acts as a switch
Combined to implement logic functions

- AND, OR, NOT

Combined to build higher-level structures

- Adder, multiplexer, decoder, register, ...


Combined to build processor

- LC-3

3-3

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Simple Switch Circuit

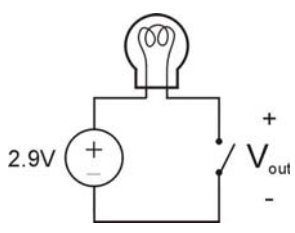

Switch open:

- No current through circuit
- Light is **off**
- V_{out} is **+2.9V**

Switch closed:

- Short circuit across switch
- Current flows
- Light is **on**
- V_{out} is **0V**

Switch-based circuits can easily represent two states: on/off, open/closed, voltage/no voltage.

3-4

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.


N-type MOS Transistor

MOS = Metal Oxide Semiconductor

- two types: N-type and P-type

N-type

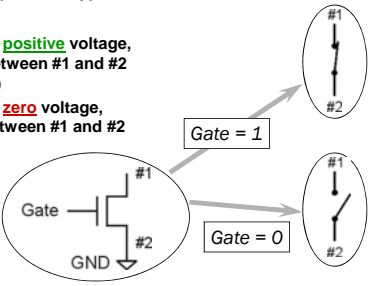- when Gate has **positive** voltage, short circuit between #1 and #2 (switch **closed**)
- when Gate has **zero** voltage, open circuit between #1 and #2 (switch **open**)



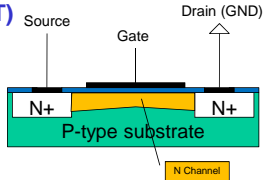

Terminal #2 must be connected to GND (0V).

3-5

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Planar N-type Metal-Oxide Semiconductor Field Effect Transistor (MOSFET)

- Start with silicon substrate on wafer
- "Dope" to create P and N wells/regions
 - Channel conducts only if electric field is present
- Overlay SiO₂ insulator
- Deposit metal (or polysilicon) gates, contacts
- Use **photolithography**
 - Project geometric shape to etch photoresist
 - Apply dopants, metal vapor
 - Repeat for each layer/component


3-6

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

P-type MOS Transistor

P-type is **complementary** to N-type

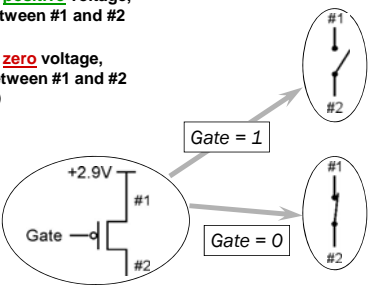- when Gate has **positive** voltage, open circuit between #1 and #2 (switch **open**)
- when Gate has **zero** voltage, short circuit between #1 and #2 (switch **closed**)



Terminal #1 must be connected to +2.9V.

3-7


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Logic Gates

Use switch behavior of MOS transistors to implement logical functions: AND, OR, NOT.

Digital symbols:

- recall that we assign a range of analog voltages to each digital (logic) symbol



- assignment of voltage ranges depends on electrical properties of transistors being used
 - typical values for "1": +5V, +3.3V, +2.9V, +1.1V
 - for purposes of illustration, we'll use +2.9V

3-8

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

CMOS Circuit

Complementary MOS

Uses both **N-type** and **P-type** MOS transistors


- P-type**
 - Attached to + voltage
 - Pulls output voltage UP when input is zero
- N-type**
 - Attached to GND
 - Pulls output voltage DOWN when input is one

For all inputs, make sure that output is either connected to GND or to +, but not both!

3-9

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.


Inverter (NOT Gate)

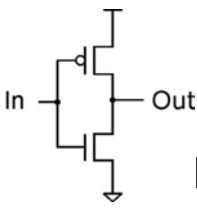

Truth table

| In | Out |
|-------|-------|
| 0 V | 2.9 V |
| 2.9 V | 0 V |


| In | Out |
|----|-----|
| 0 | 1 |
| 1 | 0 |

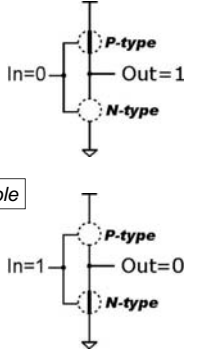

3-10

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

NOR Gate

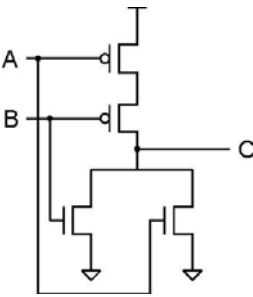


| A | B | C |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |

Note: Serial structure on top, parallel on bottom.

3-11

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.







OR Gate

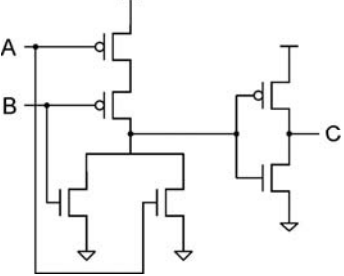

| A | B | C |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

Add inverter to NOR.


3-12

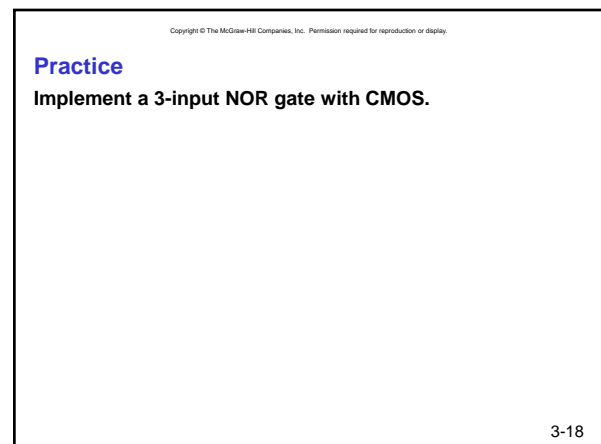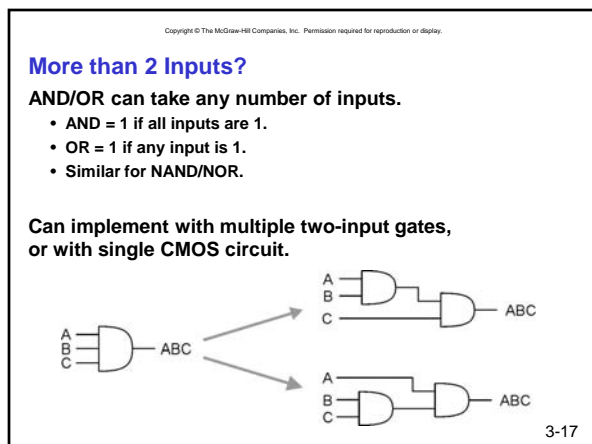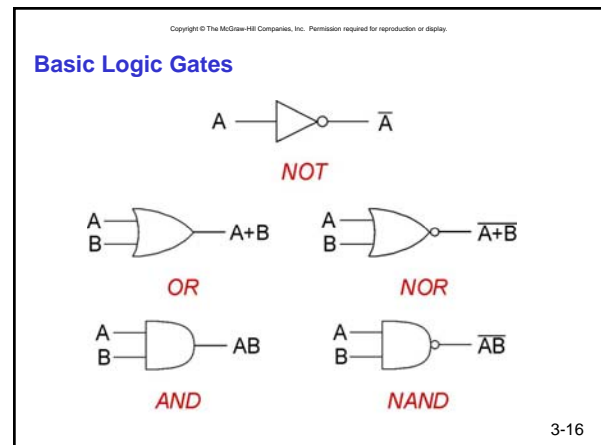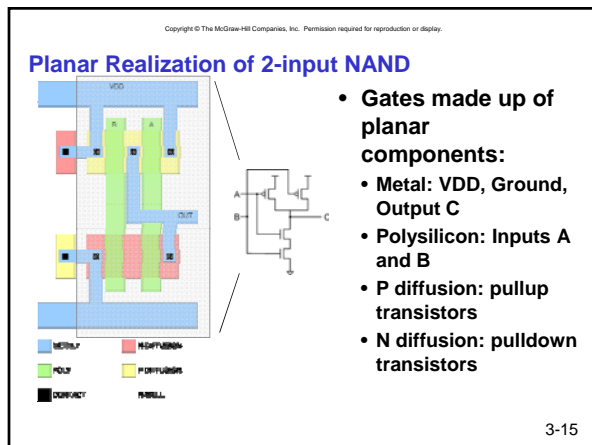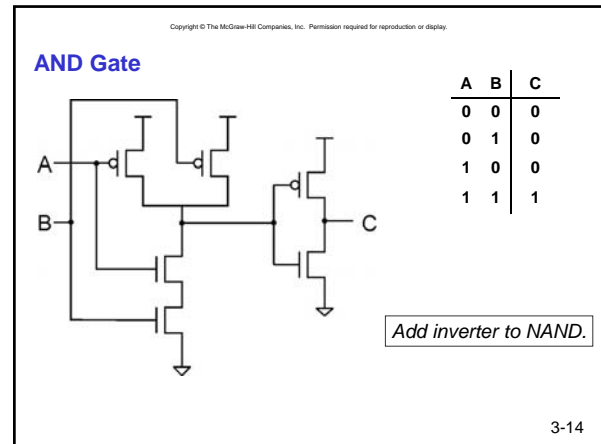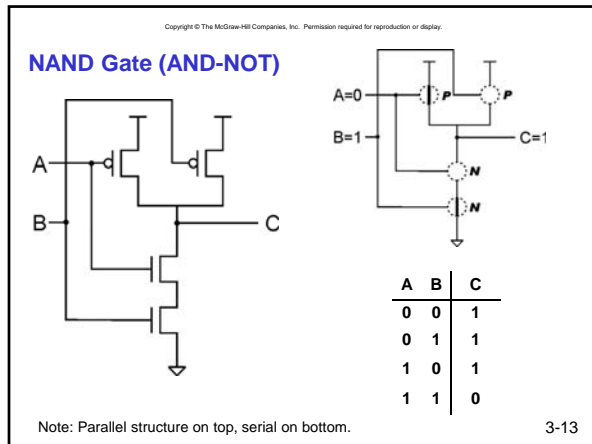

Logical Completeness

Can implement **ANY** truth table with AND, OR, NOT.

| A | B | C | D |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 0 |

 

1. AND combinations that yield a "1" in the truth table.

2. OR the results of the AND gates.

3-19

Practice

Implement the following truth table.

| A | B | C |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

3-20

DeMorgan's Law

Converting AND to OR (with some help from NOT)

Consider the following gate:



| A | B | \bar{A} | \bar{B} | $\bar{A} \cdot \bar{B}$ | $\overline{A \cdot B}$ |
|---|---|-----------|-----------|-------------------------|------------------------|
| 0 | 0 | 1 | 1 | 1 | 0 |
| 0 | 1 | 1 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 0 | 1 |

Same as $A+B$!

To convert AND to OR
(or vice versa),
invert inputs and output.

3-21

Summary

MOS transistors are used as switches to implement logic functions.

- N-type: connect to GND, turn on (with 1) to pull down to 0
- P-type: connect to +2.9V, turn on (with 0) to pull up to 1

Basic gates: NOT, NOR, NAND

- Logic functions are usually expressed with AND, OR, and NOT

Properties of logic gates

- Completeness
 - can implement any truth table with AND, OR, NOT
- DeMorgan's Law
 - convert AND to OR by inverting inputs and output

3-22

Building Functions from Logic Gates

We've already seen how to implement truth tables using AND, OR, and NOT -- an example of **combinational logic**.

Combinational Logic Circuit

- output depends only on the current inputs
- stateless

Sequential Logic Circuit

- output depends on the sequence of inputs (past and present)
- stores information (state) from past inputs


We'll first look at some useful combinational circuits, then show how to use sequential circuits to store information.

3-23

Decoder

n inputs, 2^n outputs

 - exactly one output is 1 for each possible input pattern



3-24

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Multiplexer (MUX)

n -bit selector and 2^n inputs, one output

- output equals one of the inputs, depending on selector

4-to-1 MUX

3-25

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Full Adder

Add two bits and carry-in, produce one-bit sum and carry-out.

| A | B | C _{in} | S | C _{out} |
|---|---|-----------------|---|------------------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

3-26

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Four-bit Adder

3-27

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Combinational vs. Sequential

Combinational Circuit

- always gives the same output for a given set of inputs
 - ex: adder always generates sum and carry, regardless of previous inputs

Sequential Circuit

- stores information
- output depends on stored information (state) plus input
 - so a given input might produce different outputs, depending on the stored information
- example: ticket counter
 - advances when you push the button
 - output depends on previous state
- useful for building "memory" elements and "state machines"

3-28

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

R-S Latch: Simple Storage Element

R is used to "reset" or "clear" the element – set it to zero.
S is used to "set" the element – set it to one.

If both R and S are one, out could be either zero or one.

- "quiescent" state -- holds its previous value
- note: if a is 1, b is 0, and vice versa

3-29

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Clearing the R-S latch

Suppose we start with output = 1, then change R to zero.

Output changes to zero.

Then set R=1 to "store" value in quiescent state.

3-30

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Setting the R-S Latch

Suppose we start with output = 0, then change S to zero.

Output changes to one.

Then set $S=1$ to "store" value in quiescent state.

3-31

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

R-S Latch Summary

$R = S = 1$

- hold current value in latch

$S = 0, R = 1$

- set value to 1

$R = 0, S = 1$

- set value to 0

$R = S = 0$

- both outputs equal one
- final state determined by electrical properties of gates
- Don't do it!

3-32

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Gated D-Latch

Two inputs: D (data) and WE (write enable)

- when **WE = 1**, latch is set to **value of D**
 - $S = \text{NOT}(D), R = D$
- when **WE = 0**, latch holds **previous value**
 - $S = R = 1$

3-33

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Register

A register stores a multi-bit value.

- We use a collection of D-latches, all controlled by a common WE.
- When $WE=1$, n-bit value D is written to register.

3-34

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Representing Multi-bit Values

Number bits from right (0) to left (n-1)

- just a convention -- could be left to right, but must be consistent

Use brackets to denote range:
 $D[l:r]$ denotes bit l to bit r, from *left to right*

$A = \overset{15}{0} \overset{14}{1} \overset{13}{0} \overset{12}{1} \overset{11}{0} \overset{10}{0} \overset{9}{1} \overset{8}{1} \overset{7}{0} \overset{6}{1} \overset{5}{0} \overset{4}{1} \overset{3}{0} \overset{2}{1} \overset{1}{0} \overset{0}{1}$

$A[14:9] = 101001$ $A[2:0] = 101$

May also see $A<14:9>$, especially in hardware block diagrams.

3-35

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Memory

Now that we know how to store bits, we can build a memory – a logical $k \times m$ array of stored bits.


Address Space:
 number of locations
 (usually a power of 2)

$k = 2^n$ locations

Addressability:
 number of bits per location
 (e.g., byte-addressable)

m bits

3-36

 

More Memory Details

This is not the way actual memory is implemented.

- fewer transistors, much more dense, relies on electrical properties

But the logical structure is very similar.

- address decoder
- word select line
- word write enable

Two basic kinds of **RAM** (Random Access Memory)

Static RAM (SRAM)


- fast, not very dense (bitcell is a latch)

Dynamic RAM (DRAM)

- slower but denser, bit storage must be periodically refreshed
- each bitcell is a capacitor (like a leaky bucket) that decays

Also, non-volatile memories: ROM, PROM, flash, ...



3-38

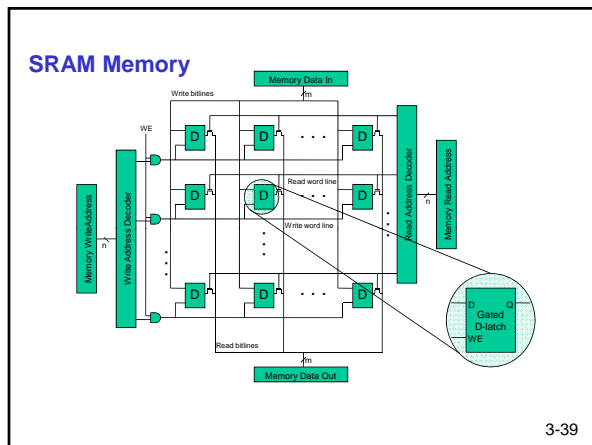

State Machine

Another type of sequential circuit

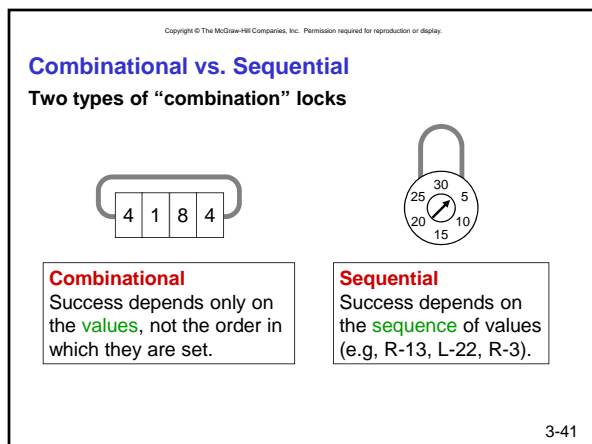 - Combines combinational logic with storage
- “Remembers” state, and changes output (and state) based on **inputs** and **current state**



State

The **state** of a system is a **snapshot** of **all the relevant elements** of the system at the moment the snapshot is taken.

Examples:

- The state of a basketball game can be represented by the scoreboard.
 - Number of points, time remaining, possession, etc.
- The state of a tic-tac-toe game can be represented by the placement of X's and O's on the board.

3-42

State of Sequential Lock


Our lock example has four different states, labelled A-D:

- A:** The lock is **not open**, and no relevant operations have been performed.
- B:** The lock is **not open**, and the user has completed the **R-13** operation.
- C:** The lock is **not open**, and the user has completed **R-13**, followed by **L-22**.
- D:** The lock is **open**.

3-43

State Diagram

 Shows **states** and **actions** that cause a **transition** between states.



3-44

Finite State Machine

A description of a system with the following components:

1. A finite number of **states**
2. A finite number of external **inputs**
3. A finite number of external **outputs**
4. An explicit specification of all **state transitions**
5. An explicit specification of what causes each external **output value**.


Often described by a state diagram.

- Inputs may cause state transitions.
- Outputs are associated with each state (or with each transition).

3-45

The Clock

 Frequently, a **clock circuit** triggers transition from one state to the next.



At the beginning of each clock cycle, state machine makes a transition, based on the current state and the external inputs.

- Not always required. In lock example, the input itself triggers a transition.

3-46


Implementing a Finite State Machine

Combinational logic

- Determine outputs and next state.

Storage elements


- Maintain state representation.

 

3-47

Storage: Master-Slave Flipflop

 A pair of gated D-latches, to isolate **next** state from **current** state.



During 1st phase (clock=1), previously-computed state becomes **current** state and is sent to the logic circuit.

During 2nd phase (clock=0), **next** state, computed by logic circuit, is stored in Latch A.

3-48

Storage

Each master-slave flipflop stores one state bit.

The number of storage elements (flipflops) needed is determined by the number of states (and the representation of each state).

Examples:


- Sequential lock
 - Four states – two bits
- Basketball scoreboard
 - 7 bits for each score, 5 bits for minutes, 6 bits for seconds, 1 bit for possession arrow, 1 bit for half, ...

3-49

Complete Example


A blinking traffic sign

 - No lights on
- 1 & 2 on
- 1, 2, 3, & 4 on
- 1, 2, 3, 4, & 5 on
- (repeat as long as switch is turned on)



3-50

Traffic Sign State Diagram

 

Transition on each clock cycle.

3-51

Traffic Sign Truth Tables

Outputs (depend only on state: S_1S_0)

| S_1 | S_0 | Z | Y | X |
|-------|-------|---|---|---|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |


Next State: $S_1'S_0'$ (depend on state and input)

| In | S_1 | S_0 | S_1' | S_0' |
|----|-------|-------|--------|--------|
| 0 | X | X | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 0 |

Whenever $In=0$, next state is 00.

3-52

Traffic Sign Logic

 

3-53

From Logic to Data Path

The data path of a computer is all the logic used to process information.

- See the data path of the LC-2 on next slide.

Combinational Logic


- Decoders -- convert instructions into control signals
- Multiplexers -- select inputs and outputs
- ALU (Arithmetic and Logic Unit) -- operations on data

Sequential Logic

- State machine -- coordinate control signals and data movement
- Registers and latches -- storage elements

3-54

LC-2/LC-3 Data Path

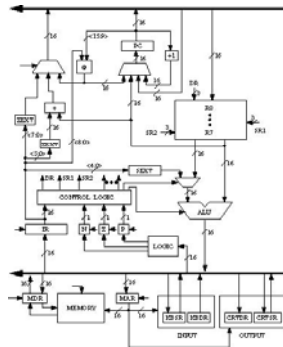

3-55